

# Ripple Carry Adder

Aman Agarwal  
Ramu Pittala


IIT Hyderabad

March 8, 2019

# Introduction


- ▶ One ripple carry adder consists of four full adders.
- ▶ Performs arithmetic sum of two binary numbers.
- ▶ All full adders are cascaded with carry output of one connected to the carry input of another.
- ▶ Multiple full adders can be cascaded to perform N-bit addition.
- ▶ Suitable for small bit applications.

### A 4 BIT RIPPLE CARRY ADDER

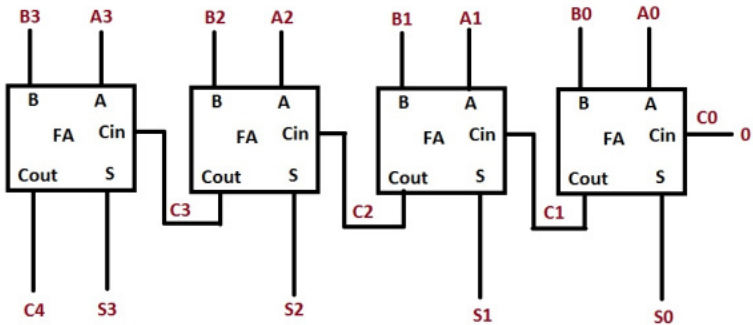

FA - Full Adders  
B - Data 2  
C - Carry

A - Data 1  
S - Sum

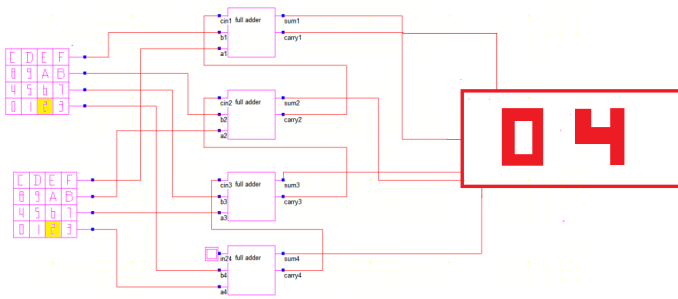

## Uses:

- ▶ Various mathematical operations can be performed like addition, subtraction etc.
- ▶ Used in ALU of various processors like ARM1.